

(1) slew rate : $SR = \frac{dV_o}{dt} \text{ V/}\mu\text{s}$



(2) $CMRR = \frac{A_d}{A_c} \Rightarrow CMRR(\text{dB}) = 20 \log_{10} \left\{ \frac{A_d}{A_c} \right\} \text{ dB}$

negative feedback

(1) open loop gain of the opamp is very high 2×10^5 for 741C
 ↓
 unsuitable for LDC

(2) not stable & varies with temperature.

Virtual Ground Concept:

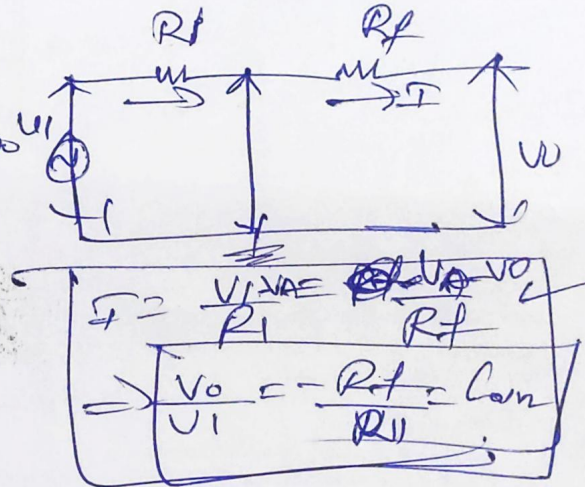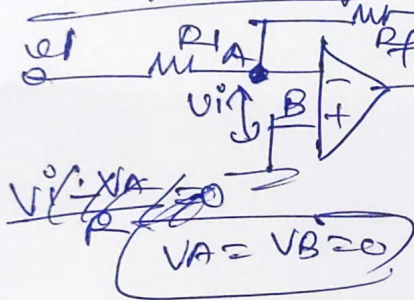

if $V_o = -10\text{V}$

$A_v = 20,000$

$\Rightarrow A_v = \frac{V_o}{V_{in}}$


$V_{in} = \frac{-10}{20,000} = 0.5 \text{ mV}$

If $A_v = 1 \Rightarrow V_{in} = 10\text{V}$

$$\frac{V_o}{V_i} = -\frac{R_f}{R_1} = \text{Gain}$$

$$\frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

(*) Inverting Amplifier:

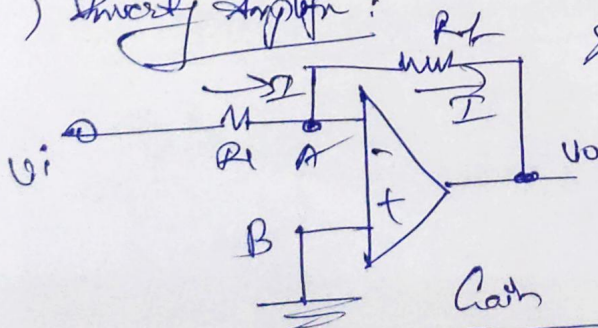

WKT $V_A = V_B$ output

$I_1 = \frac{V_i - V_A}{R_1}$ & $I_2 = \frac{V_A - V_o}{R_f}$

Equating (1) = (2)

$$\frac{V_i - V_A}{R_1} = \frac{V_A - V_o}{R_f}$$



$$\frac{V_i}{R_1} = -\frac{V_o}{R_f}$$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

if $R_1 = R_f \Rightarrow V_o = -V_i$

(2) Non-Inverting Amplifier:

9

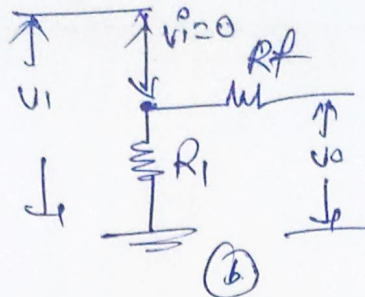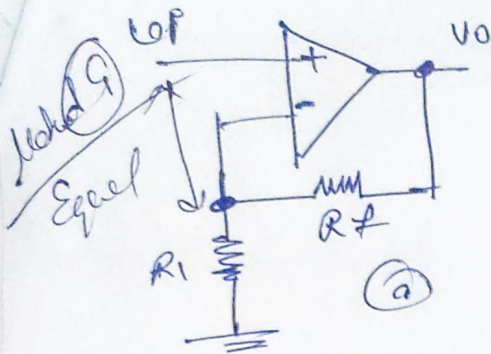


Now voltage across R_1 is $V_1 = \frac{V_o R_1}{R_1 + R_f}$

$$\Rightarrow V_o = \left(\frac{R_1 + R_f}{R_1} \right) V_1$$

$$\Rightarrow V_o = \left(1 + \frac{R_f}{R_1} \right) v_i$$

Model 2

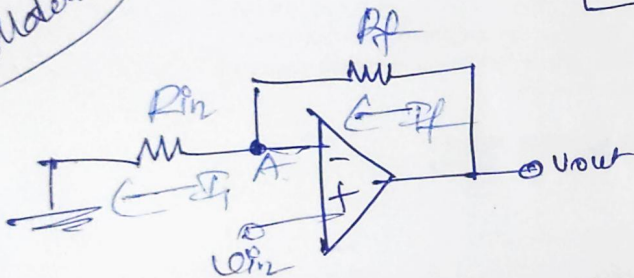

Let $V_A = V_{in}$


$$V_A = \frac{R_{in} V_{out}}{R_{in} + R_f}$$

$$\Rightarrow \frac{V_{out}}{V_A} = \frac{R_{in} + R_f}{R_{in}}$$

$$\Rightarrow V_{out} = \left(1 + \frac{R_f}{R_{in}} \right) V_A$$

$$\Rightarrow A_v = \left(1 + \frac{R_f}{R_{in}} \right)$$

Ideal op-amp negative feedback

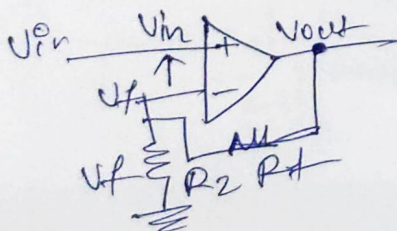


$$\text{closed loop gain} = \frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_2}$$


$$\text{feedback } \beta = \frac{V_f}{V_{out}} = \frac{R_2}{R_f + R_2}$$

(3) Unity follower / Voltage follower

(3)

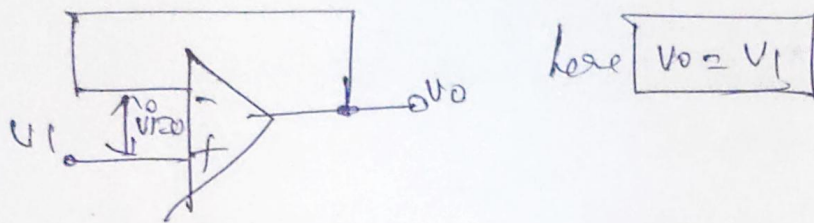

#(4) Summing Amplifier

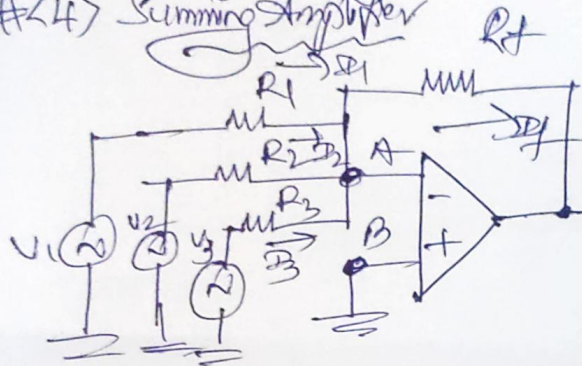


$$V_A = V_B \quad \text{KCL at node 'A'}$$

$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} + \frac{V_3 - V_A}{R_3} = \frac{V_A - V_{out}}{R_f}$$


$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{V_{out}}{R_f}$$

$$\Rightarrow V_{out} = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$
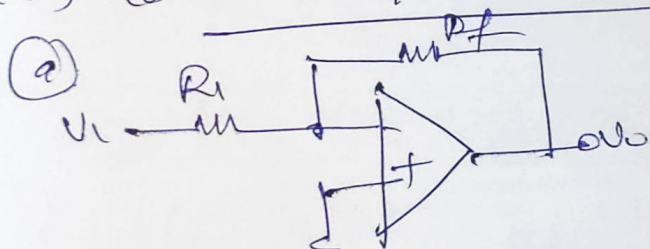
#(5) Constant Gain / fixed Gain Amplifier :




$$A = -\frac{R_f}{R_1}$$

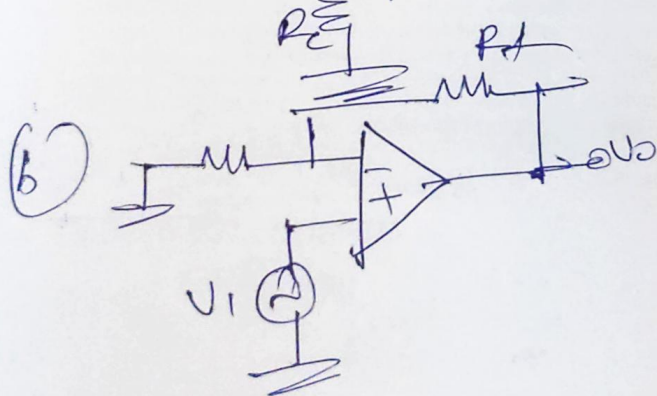

$$\Rightarrow A = 1 + \frac{R_f}{R_1}$$

#L6> Subtractor (Voltage Subtractor)

(4)

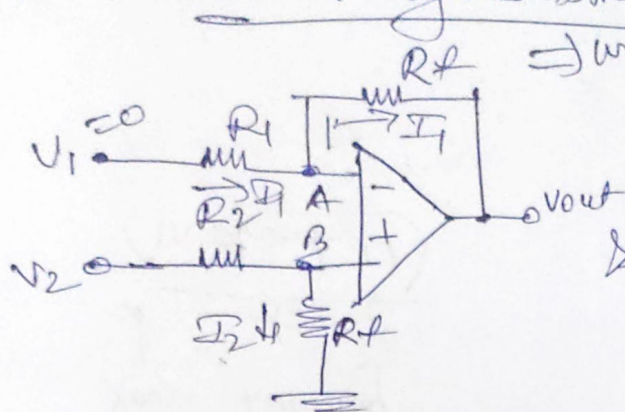

\Rightarrow We use Superposition Theorem!

Let V_{o1} be the output with V_1

& assume $V_2 = 0$

& V_{o2} be the output with V_2
assume $V_1 = 0$

Now with $V_2 = 0$, the ckt acts as an inverting amplifier & output equation is

$$V_{o1} = -\frac{R_F}{R_1} V_1 \quad (1)$$

While with $V_1 = 0$, the ckt reduces to as shown.


Let potential of node B be V_B . The potential of node A is same as B i.e. $V_A = V_B$ (Virtual short).

Apply voltage divider rule to the input V_2 loop

$$V_B = \frac{R_F}{R_2 + R_F} V_2 \quad (2)$$

from here
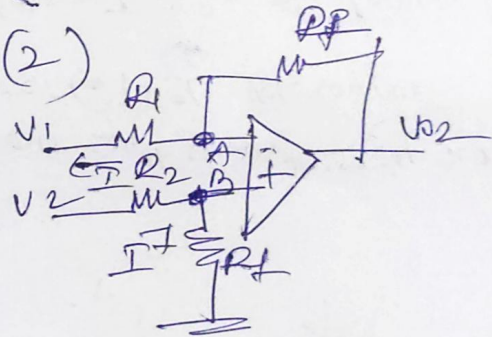
$$I_A = \frac{V_A - V_B}{R_1} = \frac{V_B - V_B}{R_1} \quad (3)$$



Now

$$I_2 = \frac{V_{o2} - V_A}{R_F} = \frac{V_{o2} - V_B}{R_F} \quad (4)$$

Equate (3) & (4)

$$\frac{V_B}{R_1} = \frac{V_{o2} - V_B}{R_F}$$

$$\Rightarrow V_{o2} = \left(\frac{R_1 + R_F}{R_1} \right) V_B$$

$$\Rightarrow V_{o2} = \left[1 + \frac{R_F}{R_1} \right] V_B \quad (5)$$

Substitute V_B from (2) in (5)

$$\Rightarrow V_{o2} = \left[1 + \frac{R_F}{R_1} \right] \left[\frac{R_F}{R_2 + R_F} \right] V_2$$

Now use Superposition theorem

$$V_o = V_{o1} + V_{o2}$$

$$\Rightarrow V_o = -\frac{R_F}{R_1} V_1 + \left[1 + \frac{R_F}{R_1} \right] \left[\frac{R_F}{R_2 + R_F} \right] V_2$$

If $R_1 = R_2$



$$V_o = \frac{R_F}{R_1} (V_2 - V_1) \quad (6)$$

If $R_1 = R_F$

$$V_o = V_2 - V_1 \quad (7)$$

#(2) Integrator:

(5)

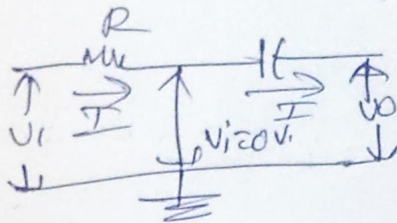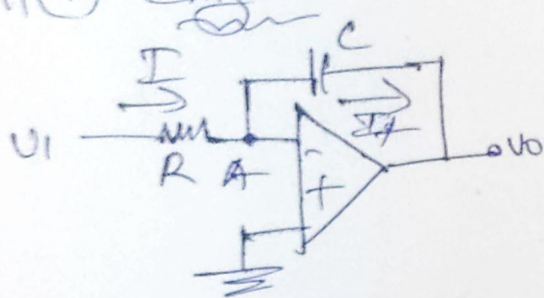

Applying KCL at node A, $I = I_f$ — (1)


where $I = \frac{V_1 - V_A}{R}$ & $I_f = C \frac{d(V_A - V_0)}{dt}$

$V_A = 0$ due to virtual ground \rightarrow (2)

$$\& \frac{V_1}{R} = C \frac{d(-V_0)}{dt} \Rightarrow \boxed{\frac{dV_0}{dt} = -\frac{1}{RC} V_1} \quad (3)$$

$$\Rightarrow \boxed{V_{out}(t) = -\frac{1}{RC} \int_0^t V_{in}(t) dt} \quad (4)$$

#(3) Differentiator:

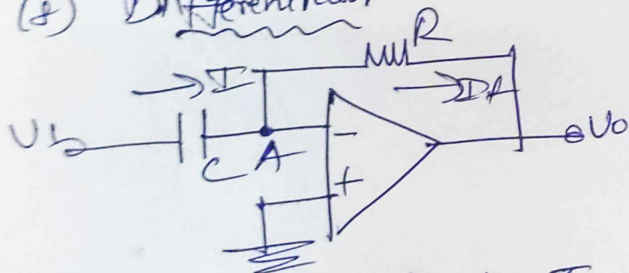

Apply KCL at node A, $I = I_f$ — (1)

$$C \frac{d(V_1 - V_A)}{dt} = \left(\frac{V_A - V_0}{R} \right) \quad (2)$$

& $V_A = 0$ due to virtual ground

$$\Rightarrow \frac{C dV_1}{dt} = -\frac{V_0}{R} \quad (3)$$

$$\Rightarrow \boxed{V_0 = -RC \frac{dV_1}{dt}} \quad (4)$$